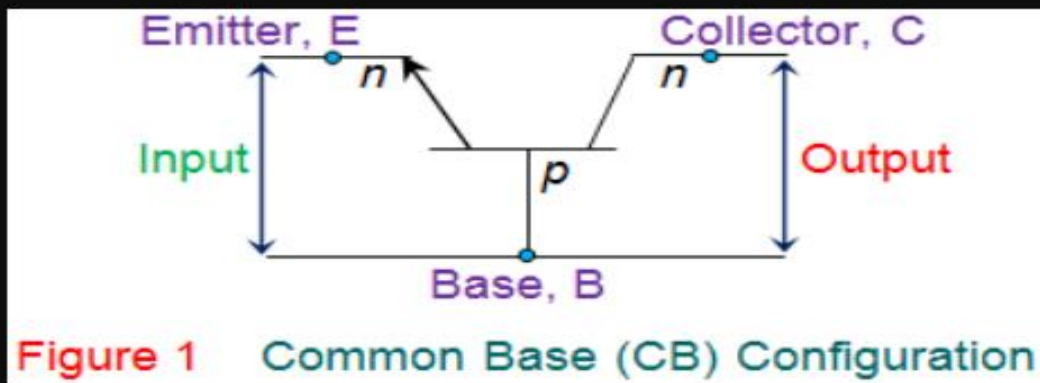


# ## COMMON BASE(CB) CONFIGURATION



- *The common base configuration for the N-P-N Transistor is shown in image.*
- *In common base configuration, emitter is the input terminal, collector is the output terminal, and base is the common terminal between input and output.*
- *As shown in figure EB junction is forward biased and CB junction is reverse bias.*
- *The input voltage is  $V_{EB}$  and input current is  $I_E$ .*
- *And The output is taken between Collector and base, Therefore the output voltages is  $V_{CB}$  and the output current is  $I_C$ .*

➤ **CURRENT AMPLIFICATION FACTOR( $\alpha$ ):**

*The current amplification factor is the relation between output current and total input current. For CB Configuration input current is  $I_E$  and output current is  $I_C$ .*

So,

$$\alpha = I_C/I_E \dots \dots \dots (1)$$

*The value of  $\alpha$  for CB configuration will always be less than 1.*

$$\text{This is because } I_C < I_E \dots \dots \dots (2)$$

➤ **Collector Current  $I_C$ :**

$$\text{Collector Current can be written as } I_C = \alpha I_E \dots \dots \dots (3)$$

➤ **Emitter Current  $I_E$ :**

*-We know that Emitter current is sum of Base current and Collector current So,*

$$I_E = I_C + I_B \dots \dots \dots (4)$$

Therefore :

$$\text{Base current is } I_B = I_E - I_C \dots \dots \dots (5)$$

Now, putting the value of (3) in (5) so,


$$I_B = I_E - \alpha I_E$$

$$I_B = I_E(1 - \alpha) \dots \dots \dots (a)$$
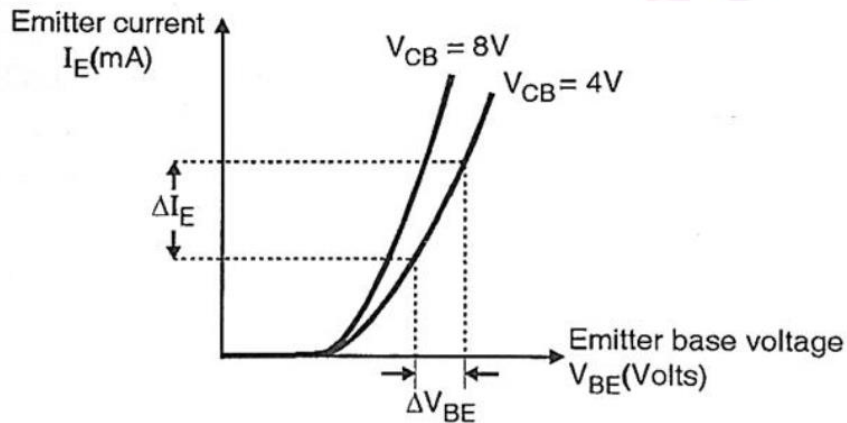
## # INPUT CHARACTERISTICS:

- *Input Characteristics is the relation between transistor input current  $I_E$  and input voltage  $V_{BE}$ , keeping the output voltage  $V_{CB}$  constant.*


- The emitter base voltage ( $V_{BE}$ ) is plotted on the X-axis and Emitter Current  $I_E$  is plotted on the Y-axis.



#### BASE WIDTH MODULATION/ EARLY EFFECT:

- IN CB CONFIGURATION OF TRANSISTOR, IF WE INCREASE  $V_{CB}$ , THEN DEPLETION LAYER AT CB JUNCTION WILL INCREASE, WHICH RESULTS IN DECREASE IN EFFECTIVE BASE WIDTH.
- Hence, concentration gradient at EB junction will increase which allows more electron from emitter to diffuse into the base.
- So, emitter current  $I_E$  will increase. Thus, when collector base voltage  $V_{CB}$  is increased, emitter current will also increase.

## # OUTPUT CHARACTERISTICS:

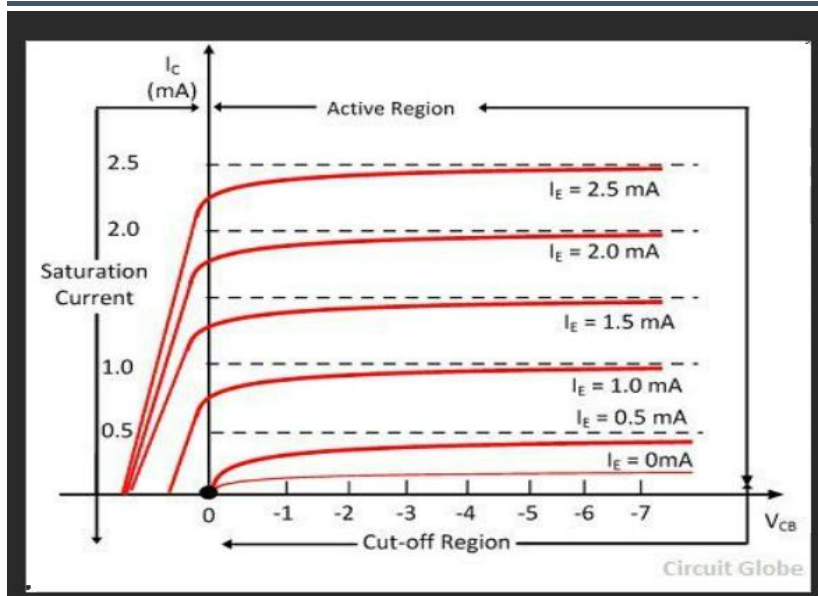

- **Output characteristics is the relation between transistor output current  $I_C$  and output voltage  $V_{CB}$  , keeping the input current  $I_E$  constant.**

**( 1) A transistor can operate in any of three region of operation.**

- (i) Cutoff region**
- (ii) Active region and**
- (iii) Saturated region**

**As reverse bias voltage  $V_{CB}$  is increase. Collector-base depletion region also increase If an expensive reverse-bias voltage is applied then collector-base depletion region penetrating into the base until it makes contact with emitter base depletion region.**